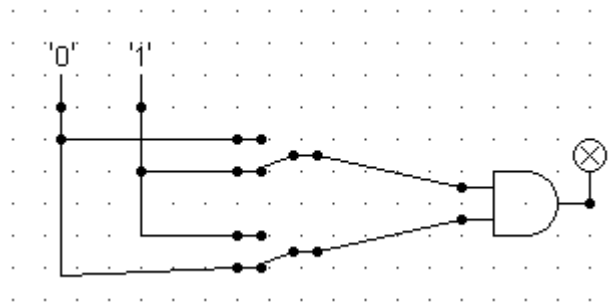


1. Draw the logic diagram of the following gates using logsim and complete the Truth tables.


a) AND

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1




b) NOR (do the same as in Q No a for all of the following)

A	B	(A + B)'
0	0	1
0	1	0
1	0	0
1	1	0

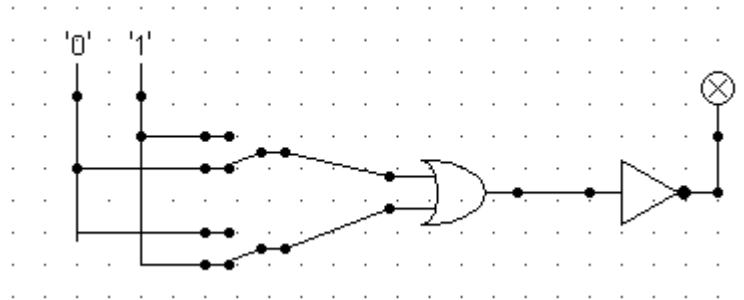


c) OR

A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

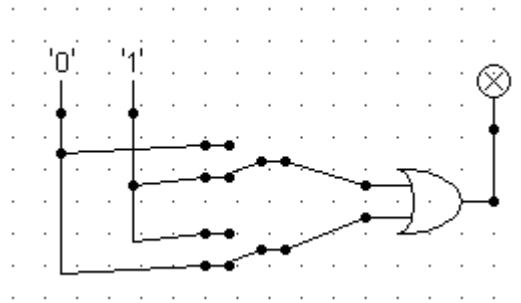


d) NAND (using NOT and AND)

A	B	$(A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

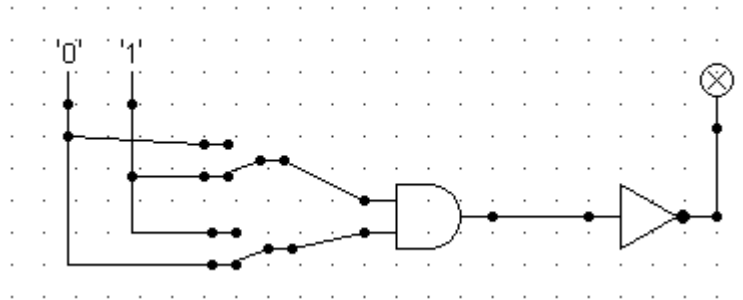


e) XOR using AOI

A	B	$A'B+AB'$
0	0	0
0	1	1
1	0	1
1	1	0

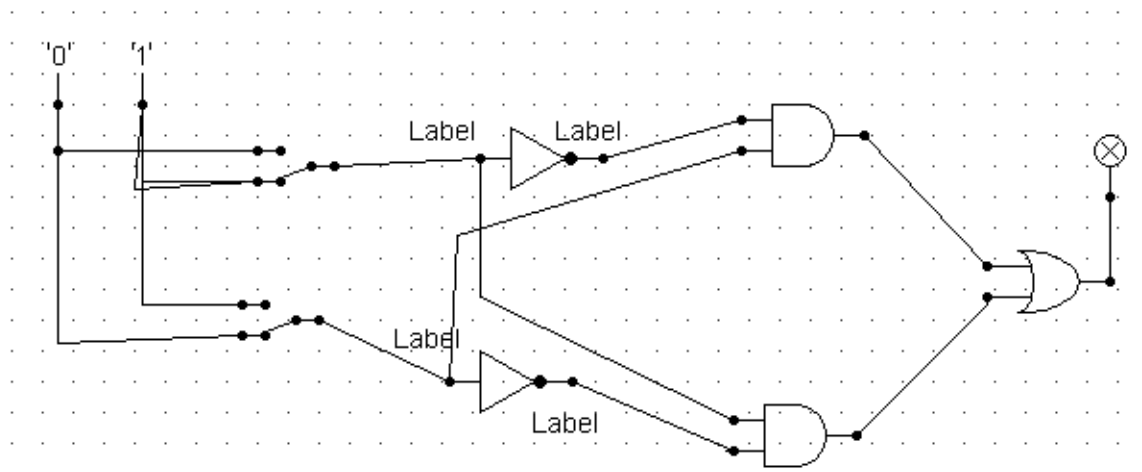


2. Use LogSim to build the equivalent circuit for the following Boolean equations.

A	B	$\neg(A+B)$	$\neg A \cdot \neg B$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

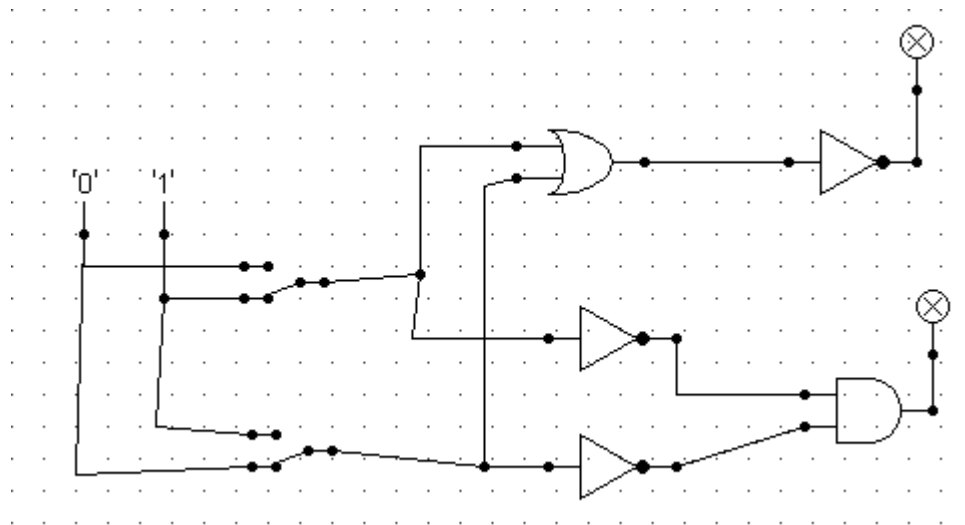


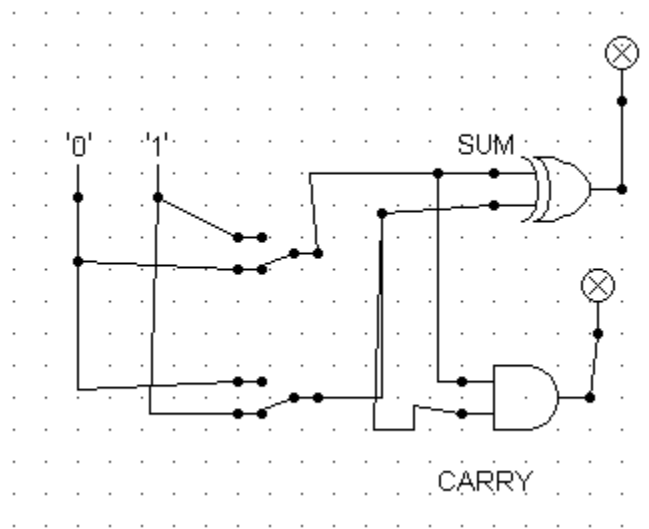3. Draw the following circuit of half adder using LogSim.




4. Draw full adder using Logsim and construct truth table.

A	B	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

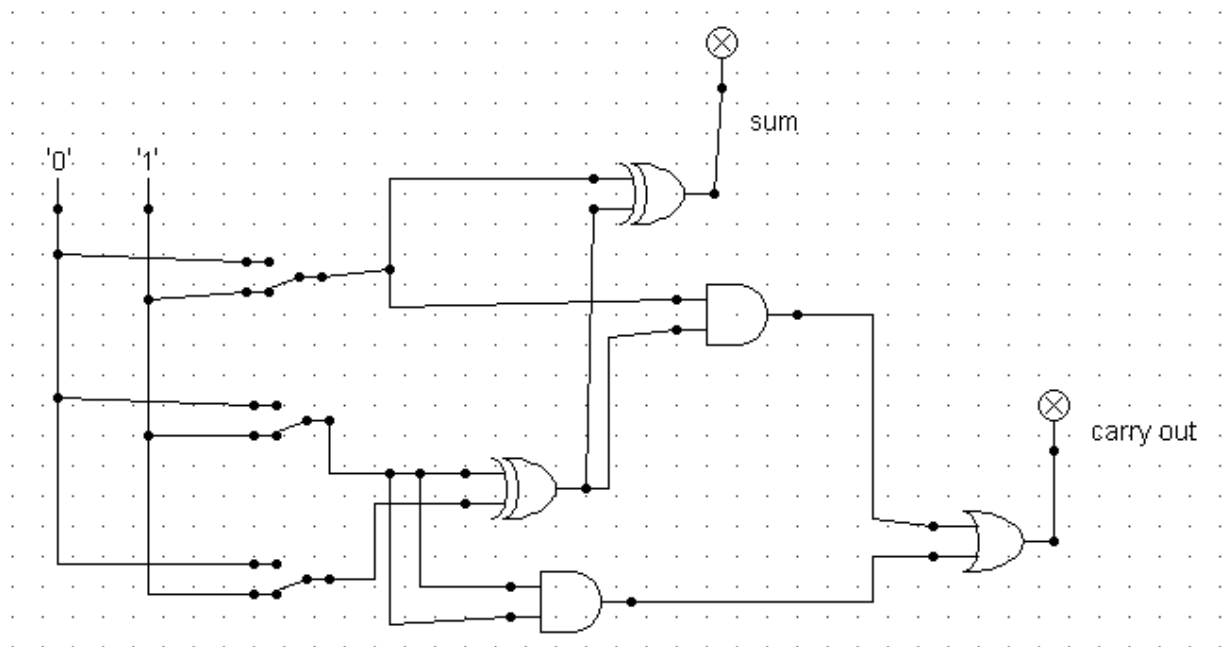


5. Draw the logic circuit for the following Boolean equations using logsim simulator.

a. $AB+C$

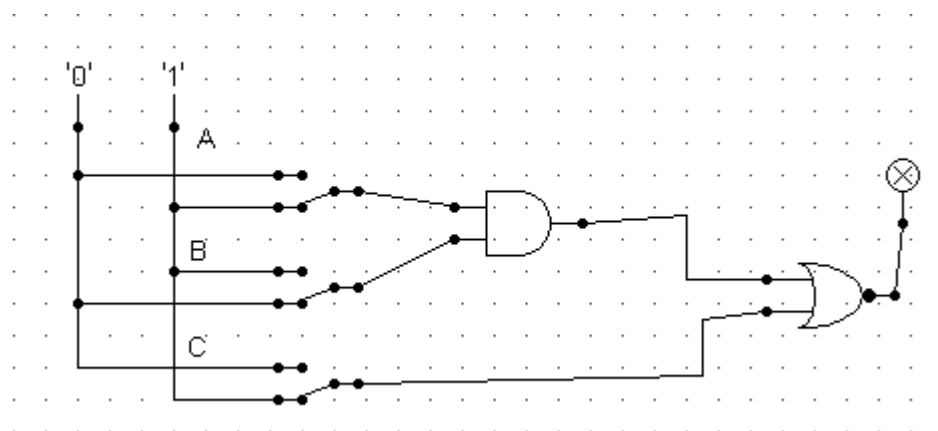

b. $A(B+C)$

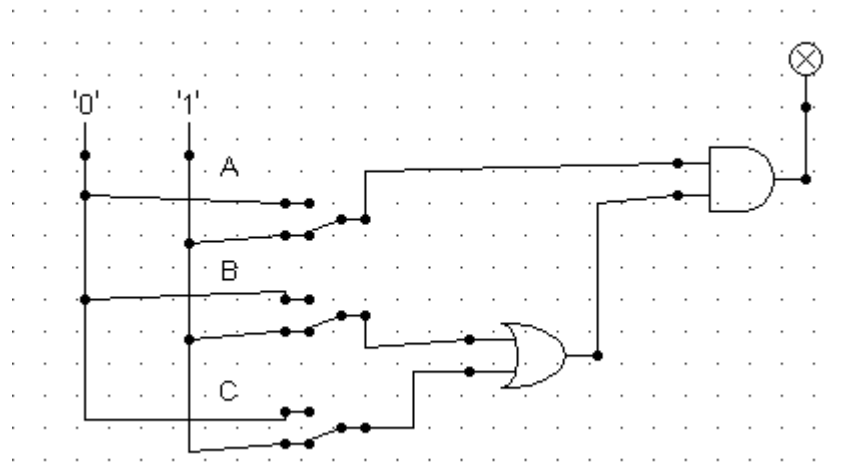

c. $X'Y'Z'$

